

FERMILAB  
ENGINEERING NOTE

SECTION

PROJECT

SERIAL-CATEGORY

PAGE

SUBJECT

NAME

DATE

REVISION DATE

6

Impedance Matching Lab.Purpose

Design, build, and test a single stub tuner matching network for matching various resistive impedances to  $50 \Omega$  at 60 MHz.

Equipment

Network Analyzer

Various mystery impedances in pumona boxes.

Assorted lengths of RG-58 cable with BNC connectors

BNC tees, bullets, and barrels

Smith Charts


Compass & ruler

Calculator

Background Info.

A single stub tuner has the following topology.

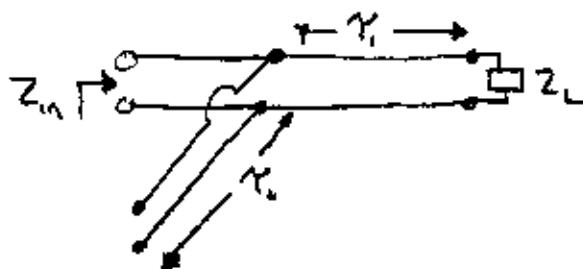See class notes for an example on how to design a single stub tuner.





FERMILAB

## ENGINEERING NOTE

SECTION

PROJECT

SERIAL-CATEGORY

PAGE

2

SUBJECT

NAME

## Impedance Matching Lab.

DATE


REVISION DATE

For a given "mystery" load:

- 1) Set the network analyzer (NWA) to measure  $S_{11}$  at a center freq. of 60 MHz with a span of 0 Hz.
- 2) The cables out of NWA should be equipped with BNC adapters.
- 3) Calibrate the  $S_{11}$  measurement with an OPEN response.
- 4) Set the display format to Smith Chart and verify that the calibration is valid by measuring an "open" and a  $50\Omega$  load.
- 5) Attach a "mystery" load to port ① and measure the complex impedance and reflection coefficient.
- 6) On a Smith Chart (on paper) determine the angle needed to rotate the reflection coefficient to the "mirror" real circle.  
There are 2 answers. See Smith Chart ①

THE EMELOID CO., INC.  
HILLSIDE, N. J.

# Smith Chart (1)

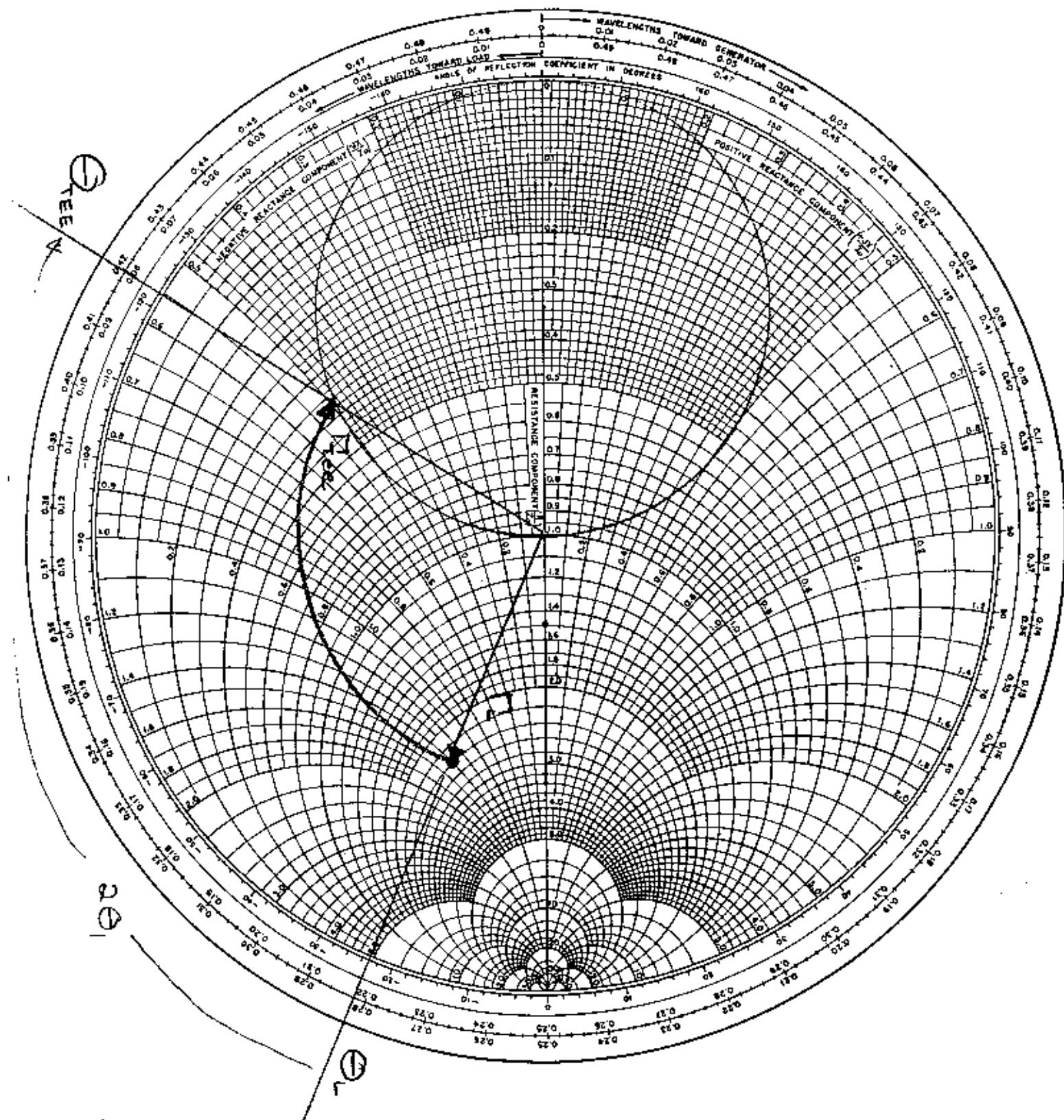

FERMILAB  
ENGINEERING NOTE

SECTION

PROJECT

SERIAL-CATEGORY

PAGE

3

SUBJECT

NAME

DATE

REVISION DATE

7) Calculate  $\gamma_i$ 

$$2\Theta_i = 360^\circ \cdot f \cdot 2\tau, \quad f = 60 \text{ MHz.}$$

8) Add a length of cable that is  $\leq \tau_i$  to the mystery load.9) Switch the NWA display to phase format and measure the phase of the  $\Gamma$  of the delayed mystery load. Add BNC Bulletts and Barrels onto the load delay cable until the phase of the reflection coefficient = the phase of  $\Gamma_{TEE}$ 10) Measure the complex impedance and  $\Gamma$  of the delayed load. Does it equal  $Z_{TEE}$  &  $\Gamma_{TEE}$ ?



FERMILAB

## ENGINEERING NOTE

SECTION

PROJECT

SERIAL-CATEGORY

PAGE

4.

SUBJECT

NAME


DATE

REVISION DATE


Impedance Matching Lab.

- 11). On Smith Chart, flip rotated impedance to the admittance chart and determine what value of <sup>imaginary</sup> admittance must be added to bring  $\Pi$  to zero. (Smith Chart 2)
- 12) On Smith Chart, determine what angle is needed to rotate the impedance of an open circuit to the value calculated in step 11. From the angle ( $2\theta_a$ ), calculate the length of cable needed to give a phase shift @ 60 Hz of  $\theta_2$  ( $r_2$ )  
(Smith Chart 3)
- 13) Remove the delayed mystery load from the NWA. Add an open circuited cable with a length  $\leq r_2$  onto port ① of the NWA. With the NWA in phase format, add BNC bullets and barrels to this cable until the phase of the reflection coefficient =  $2\theta_2$ .

# Smith Chart ②

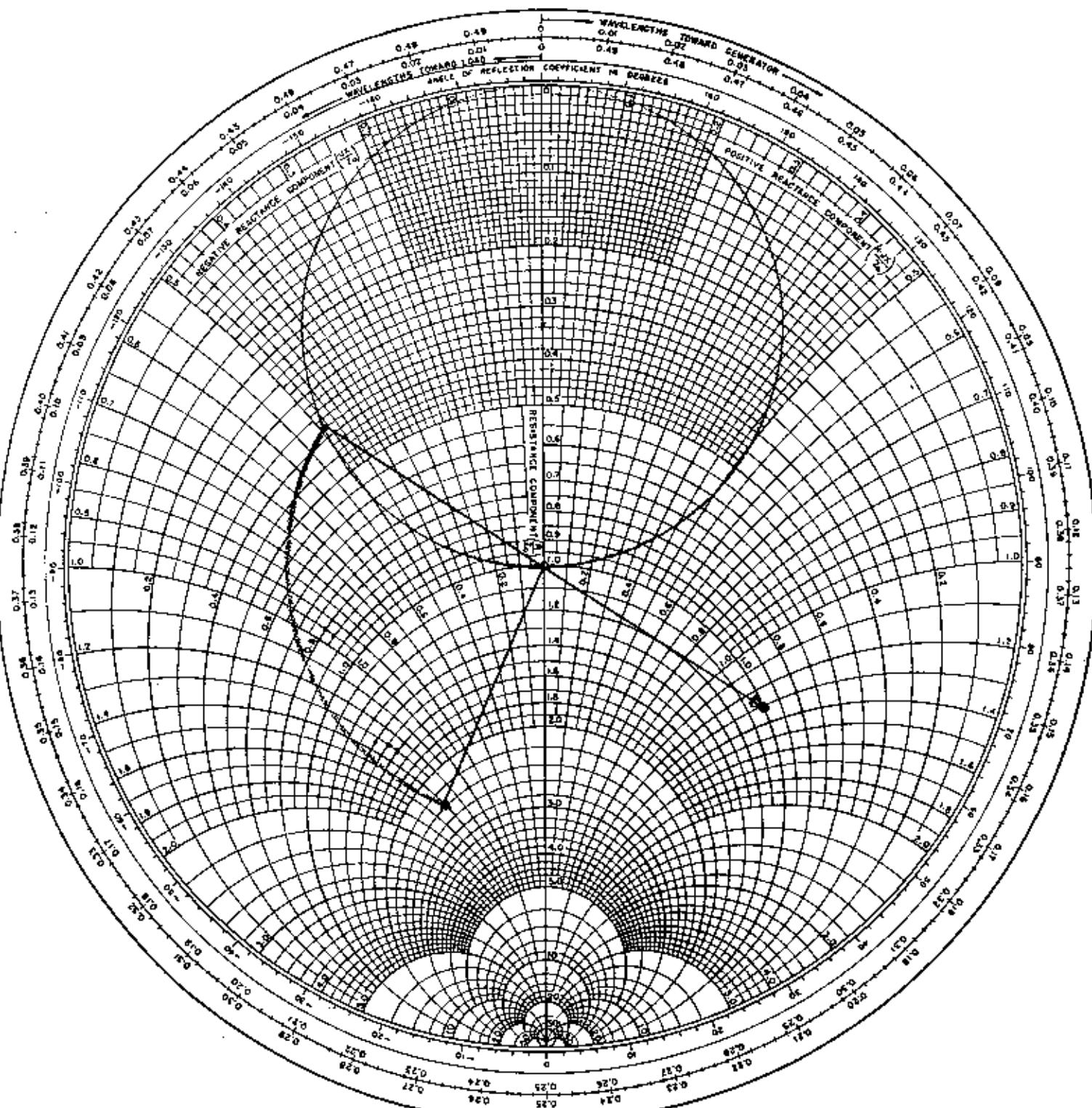

# Smith Chart (3)

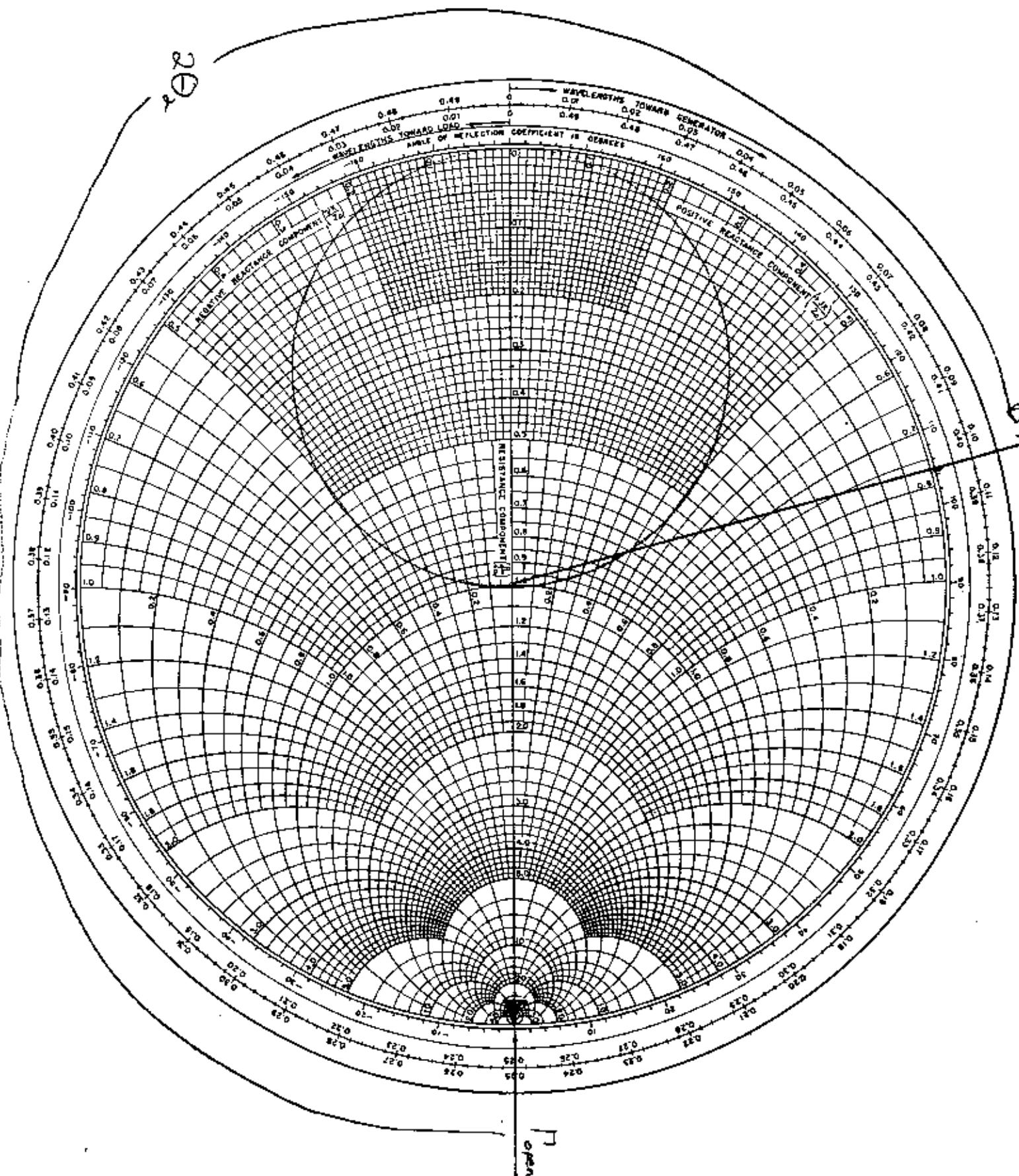



FERMILAB

## ENGINEERING NOTE

SECTION

PROJECT

SERIAL-CATEGORY

PAGE

5.

SUBJECT

NAME

Impedance Matching Lab.

DATE

REVISION DATE

- 14) Connect the delayed mystery load and the delayed open circuit together with a BNC Tee. Measure the complex impedance and reflection coefficient. Is  $Z_{\text{match}} = 50 \Omega$ ? Is  $\Gamma_{\text{match}} = 0$ ?
- 15) Set the NWA to sweep from 50 to 70 MHz. Calibrate  $S_{11}$  with an OPEN response and attach the matched load. How broad band is the match. Sketch  $\log |S_{11}|$  vs frequency. Sketch the frequency trajectory of  $S_{11}$  on a Smith Chart.
- 16) Try "tweaking" the match by adding or removing BNC barrels & bullets.
- 17) Repeat experiment for other mystery loads until you are sick of this lab.

THE ENCLOID CO., INC.  
HILLIDGE, N. J.

$$2\theta_1 = 119^\circ$$

$$\gamma_1 = 3.3 \text{ nS}$$

$$Y_P = -j1.08$$

$$Z_P = j.925$$

$$2\theta_2 = 336^\circ$$

$$\gamma_2 = 9.33 \text{ nS}$$

$$2\theta_1 = 240^\circ$$

$$\gamma_1 = 6.66 \text{ nS}$$


$$Y_P = -j1.15$$

$$Z_P = -j.87$$

$$2\theta_2 = 97.5^\circ$$

$$\gamma_2 = 2.7 \text{ nS}$$

150-12

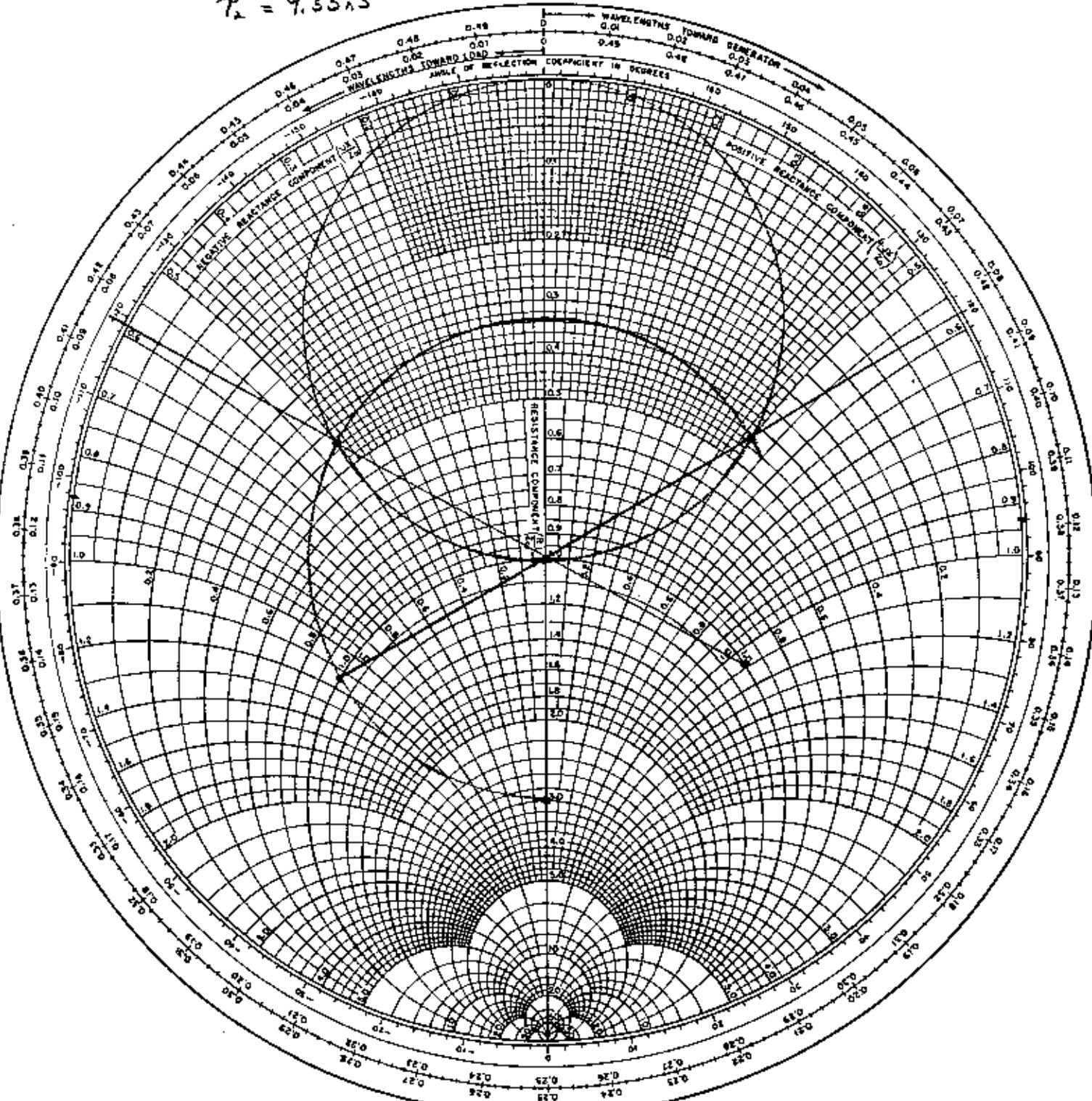

THE EMELOID CO., INC.  
MILLBROOK, N. J.

$$\begin{aligned}2\theta_1 &= 110^\circ \\ \gamma_1 &= 3.65 \text{ nS} \\ Y_P &= -j.72 \\ Z_P &= j1.39 \\ 2\theta_2 &= 288.5^\circ \\ \gamma_2 &= 8.01 \text{ nS}\end{aligned}$$

$$\begin{aligned}2\theta_1 &= 250^\circ \\ \gamma_1 &= 6.94 \text{ nS} \\ Y_P &= j.72 \\ Z_P &= -j1.4 \\ 2\theta_2 &= 71.5^\circ \\ \gamma_2 &= 1.98 \text{ nS}\end{aligned}$$

100Ω

